

# DAY 30 - 111 DAYS VERIFICATION CHALLENGE

Topic: Design FAQ's

Skill: Digital Electronics, computer architecture

BAY 30 CHALLENGE:

## 1. What is a sequence generator circuit? Application of sequence generator?

A sequence generator circuit is a digital circuit designed to generate a predefined sequence of binary numbers or states. It typically consists of flip-flops and logic gates arranged to produce the desired sequence. Sequence generators can be constructed using various methods, including shift registers, counters, or state machines.

1. **Digital Communication:**
  - PN Sequence for spread spectrum communication.
  - Scrambling/Descrambling data.
2. **Control Systems:**
  - State machines for automation (e.g., traffic lights).
3. **Testing and Verification:**
  - BIST for IC testing.
  - Pattern generation for memory tests.
4. **Cryptography:**
  - Key stream generation for encryption.
5. **Signal Processing:**
  - PCM pattern generation.
  - Digital waveform generation.
6. **Event Sequencing:**
  - Finite state machines for event control (e.g., vending machines).
7. **Data Transmission:**
  - Ensuring proper order and timing of data sequences.

## 2. What is a transmission gate in the digital circuit?

A transmission gate is a type of electronic switch used in digital circuits, commonly implemented using complementary metal-oxide-semiconductor (CMOS) technology. It consists of a parallel combination of an n-channel

MOSFET (NMOS) and a p-channel MOSFET (PMOS), controlled by complementary gate signals.

### 3. What is a pass transistor logic circuit? Advantages of using pass transistor logic.

**Pass transistor logic (PTL)** is a design technique where transistors (typically MOSFETs) are used to control the connection of signals between nodes, effectively passing logic levels directly rather than through traditional logic gates.

#### **Advantages of Pass Transistor Logic:**

- **Lower Power Consumption:** Reduced switching activity and capacitance lead to lower dynamic power consumption.
- **Higher Speed:** Fewer gate delays and more direct signal paths improve propagation speed.
- **Reduced Area:** Fewer transistors and simplified routing decrease silicon area and complexity.

### 4. Why are most interrupts active low?

**Active low interrupts** are preferred in digital circuits for several reasons:

- **Noise Immunity:** Logic low (0) is generally less susceptible to noise than logic high (1), reducing the risk of false triggering.
- **Pull-Up Resistors:** When using pull-up resistors, an unconnected or open circuit naturally reads as high, ensuring a defined state and avoiding unintended interrupts.
- **Standardization:** Many devices and protocols are designed with active low logic, promoting compatibility and standardization.

### 5. Define Pair, Quad, and Octet?

- **Pair:** A group of two items.
- **Quad:** A group of four items.
- **Octet:** A group of eight items, often used to refer to an 8-bit byte in computing.

### 6. Define Fan-in and Fan-out?

- **Fan-in:** The number of inputs a logic gate can handle. It indicates how many signals can be fed into a single gate.

- **Fan-out:** The number of inputs that a single output can drive without degrading performance. It represents how many gate inputs a single output can connect to and still maintain proper signal levels.

## 7. What is power dissipation?

**Power dissipation** refers to the process by which an electronic circuit converts electrical energy into heat. It is a measure of the power consumed by the circuit that is not used for useful work and is instead released as heat. This is crucial for ensuring the thermal management and reliability of electronic devices.

## 8. What is metastability? What are its effects?

**Metastability** occurs in digital circuits when a flip-flop or latch is unable to settle into a stable '0' or '1' state within the expected time due to a violation of setup or hold times.

### Effects of Metastability:

- **Indeterminate Outputs:** The circuit may produce unpredictable outputs, leading to incorrect operation.
- **Timing Issues:** Metastability can cause delays, leading to timing errors and system instability.
- **System Failure:** Prolonged metastable states can propagate through the system, potentially causing failures or erratic behavior.

## 9. What is an Arbiter? Explain its operation.

**An arbiter** is a digital circuit that determines which of several input signals should be granted access to a shared resource, such as a data bus or memory.

### Operation of an Arbiter:

1. **Request Detection:** The arbiter monitors multiple request signals from different sources.
2. **Priority Evaluation:** It uses a predefined priority scheme (e.g., fixed priority, round-robin) to evaluate which request to grant.
3. **Grant Signal:** The arbiter sends a grant signal to the selected source, allowing it to access the shared resource.
4. **Fairness and Deadlock Prevention:** Advanced arbiters implement fairness algorithms to prevent starvation and ensure that all sources get timely access.