


DAY 5-111 DAYS VERIFICATION CHALLENGE

Topic: Multiplexers, Demultiplexers


Skill: Digital Electronics

DAY 5 CHALLENGE:


1. Design 16:1 MUX using 2:1 MUX

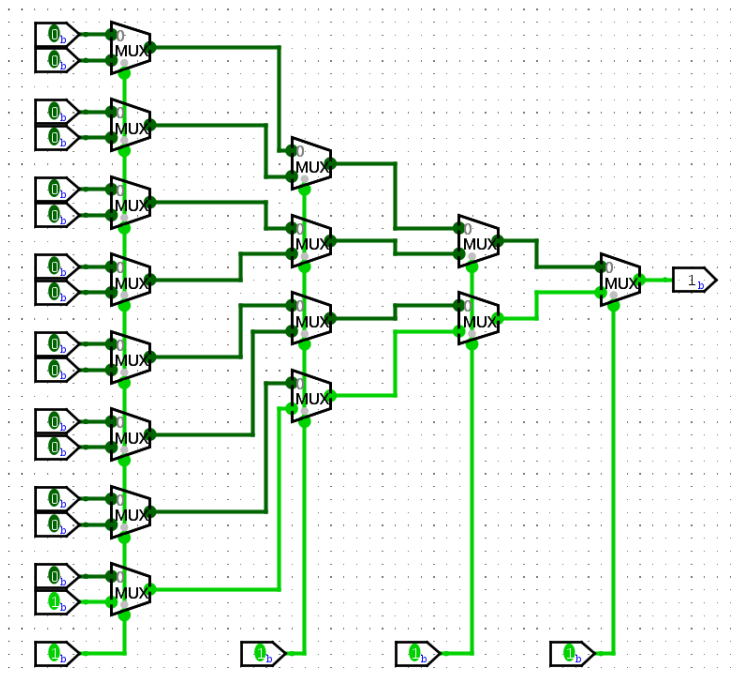


2. Design D-FF using MUX

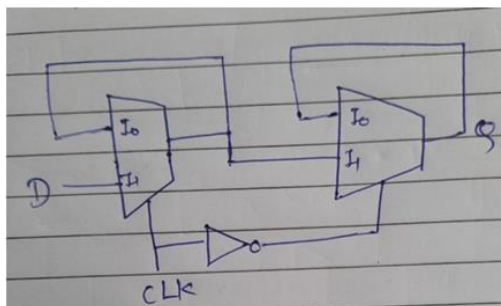

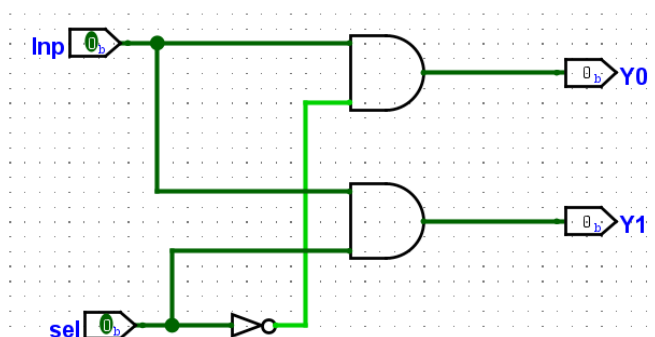3. Design a 1:2 DEMUX that can be used as an inverter & also as a buffer.



4. Design NAND Gate using 1:2 DEMUX

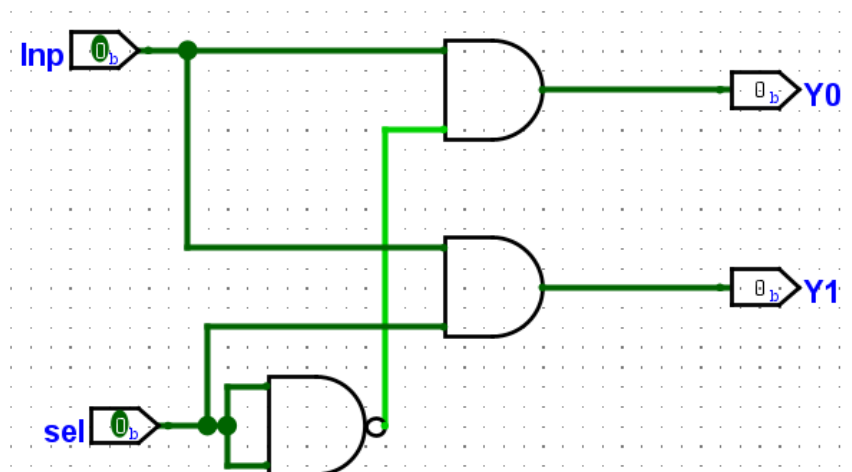

5. What is the difference between Decoder & DEMUX?

A decoder converts binary inputs to one-hot outputs with n inputs and 2^n outputs, while a DEMUX routes one data input to one of 2^n outputs based on n select lines.

6. If D0 input of a 2:1 MUX is connected to ground, what is the output ?

| Sel | D0 | D1 | Y |
|-----|-----|----|---|
| 0 | Gnd | 0 | 0 |
| 1 | Gnd | 0 | 0 |
| 0 | Gnd | 1 | 0 |
| 1 | Gnd | 1 | 1 |

7. If D1 input of 2:1 MUX is connected to 1, what is the output?

| Sel | D0 | D1 | Y |
|-----|----|------------|---|
| 0 | 0 | Constant 1 | 1 |
| 1 | 0 | Constant 1 | 0 |
| 0 | 1 | Constant 1 | 1 |
| 1 | 1 | Constant 1 | 1 |

8. List the applications of:

a. Multiplexer

- **Data Routing:** Directs multiple data sources to a single destination.
- **Communication Systems:** Combines multiple signals for transmission over one line.
- **Digital Circuits:** Selects data inputs in CPUs and memory.

- **Signal Processing:** Chooses between different signal channels.
- **Embedded Systems:** Selects inputs from multiple sensors.

b. Demultiplexer

- **Data Distribution:** Directs a single data input to multiple outputs.
- **Communication Systems:** Splits a single signal into multiple channels.
- **Digital Circuits:** Routes data to various parts of a system.
- **Display Systems:** Controls display segments.
- **Testing and Debugging:** Routes test signals to different circuit areas.