

# DAY 42 - 111 DAYS VERIFICATION CHALLENGE

Topic: Advanced verilog codes


Skill: Verilog, RTL design

DAY 42 CHALLENGE:

## 1. Design the following in Verilog:

 **A circuit that can be used as an inverter/buffer depending on the input signal INV. If INV=1, the circuit acts as an inverter. If INV=0, the circuit acts as a Buffer.**

```
module inverter_buffer(  
    input data_in,  
    input inv,  
    output reg data_out  
);  
always @(*)  
begin  
    if(inv)  
        begin  
            data_out = ~data_in ;  
        end  
    else  
        begin  
            data_out = data_in ;  
        end  
    end  
end  
endmodule
```




**2. Design a module 4bit\_adder\_subtractor\_dut which has a function 4b\_add\_sub which takes an input signal add. If add=1, the function performs addition of two 4-bit inputs 'A' & 'B', else it performs subtraction of 'A' & 'B'**

```

module add_sub(
    input add,
    input [3:0] A,
    input [3:0] B,
    output reg[4:0] out
);
always @(*)
begin
    if(add)
        out = A + B ;
    else
        out = A - B ;
    end
endmodule

```

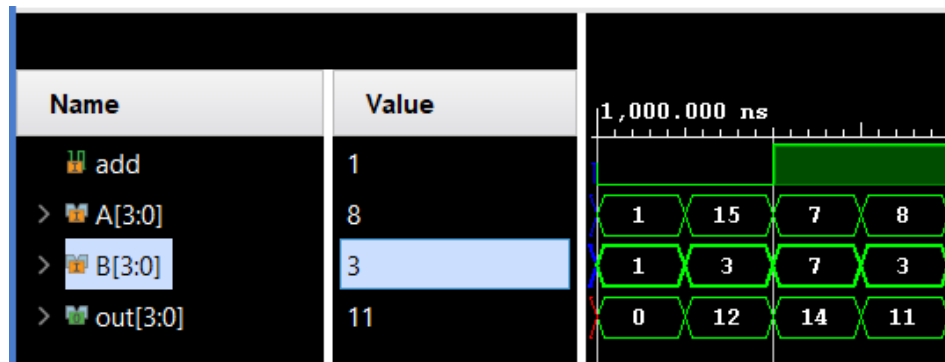

### 3. Design following using Verilog:


#### I. 3-bit Johnson Counter

```

module three_bit_johnson_cnt(
    input clk,
    input rst,
    output reg [2:0] count
);

always @(posedge clk or posedge rst)
begin
    if (rst)
        count <= 3'b000 ;
    else
        count <= {~count[0],count[2:1]};
    end
endmodule

```

 

#### II. SR latch

```


module SR_latch(
    input wire S, R,
    output reg Q, Qn

```

```

);
always @(*) begin
    if (S == 1 && R == 0) begin
        Q <= 1'b1;
        Qn <= 1'b0;
    end else if (S == 0 && R == 1) begin
        Q <= 1'b0;
        Qn <= 1'b1;
    end else if (S == 0 && R == 0) begin
        // Maintain previous state; no changes to Q and Qn
    end else if (S == 1 && R == 1) begin
        // This is typically an invalid state for an SR latch
        // Outputs remain unchanged or follow a specific
        behavior based on design choice
    end
end
endmodule

```

 

#### 4. Design an FSM in Verilog with below states:

- I. **IDLE** - This is the default state on reset.  
**IDLE** state can transition to 2 states **GRNTO** & **GRNT1**:  
**GRNTO**- if req0=1     **GRNT1**- if req1=1
- II. **GRNT 0** - This state is achieved from **IDLE** state when req0=1  
 If req0 remains '1', the state **GRNTO** state remains unchanged.  
 If req0 = 0, then **GRNTO** transitions to **IDLE** state.
- III. **GRNT 1** - This state is achieved from **IDLE** state when req1=1  
 If req1 remains '1', the state **GRNT1** state remains unchanged.  
 If req1 =0, then **GRNT1** transitions to **IDLE** state.

```

module FSM (
    input wire clk,          // Clock signal
    input wire rst,          // Reset signal
    input wire req0,         // Request signal 0
    input wire req1,         // Request signal 1
    output reg [1:0] state // Output state (encoded as 2 bits)
);

// State encoding
localparam IDLE = 2'b00;
localparam GRNTO = 2'b01;

```

```

localparam GRNT1 = 2'b10;

// State register
reg [1:0] next_state;

// Sequential logic for state transition
always @(posedge clk or posedge rst) begin
    if (rst) begin
        state <= IDLE;
    end else begin
        state <= next_state;
    end
end

// Combinational logic for next state determination
always @(*) begin
    case (state)
        IDLE: begin
            if (req0) begin
                next_state = GRNT0;
            end else if (req1) begin
                next_state = GRNT1;
            end else begin
                next_state = IDLE;
            end
        end
        GRNT0: begin
            if (req0) begin
                next_state = GRNT0; // Remain in GRNT0 if req0
is high
            end else begin
                next_state = IDLE; // Transition to IDLE if req0
goes low
            end
        end
        GRNT1: begin
            if (req1) begin
                next_state = GRNT1; // Remain in GRNT1 if req1
is high
            end else begin
                next_state = IDLE; // Transition to IDLE if req1
goes low
            end
        end
        default: next_state = IDLE; // Default to IDLE for safety
    endcase
end
endmodule

```

