

# DAY 8-111 DAYS VERIFICATION CHALLENGE

Topic: Combinational Circuits

Skill: Digital Electronics

DAY 8 CHALLENGE:

## 1. What is a Buffer? What are its applications?

A buffer is a temporary storage area, typically used to hold data while it is being moved from one place to another. It can be part of memory, a disk, or a communication system. Buffers are used to accommodate differences in the rate of data flow between two devices or processes, allowing for smoother and more efficient data handling.

**Application :**

- **Signal Isolation:** Prevent loading effects between stages.
- **Impedance Matching:** Maximize power transfer and minimize signal loss.
- **Driving Capacitive Loads:** Maintain signal integrity over long distances.
- **Bus Systems:** Control access and prevent conflicts on shared data lines.
- **Timing and Synchronization:** Introduce controlled delays for timing alignment.
- **Signal Amplification:** Boost weak signals for further processing.


## 2. What is tri-state buffers?

Tri-state buffers have an additional control line, often called the enable line. When the enable line is active, the buffer outputs the data. When the enable line is inactive, the buffer goes into the high impedance state.
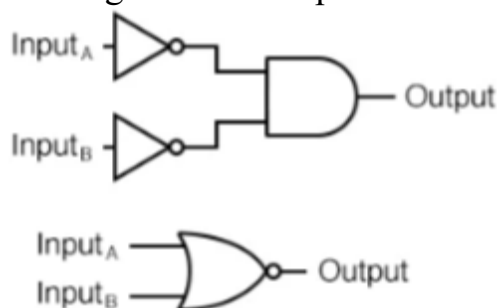
## 3. What is the difference between NAND and negative input AND gate?

A NAND gate is a fundamental digital logic gate that performs an AND operation on its inputs and then negates (inverts) the result. It has two or more inputs and one output. The output of a NAND gate is low (0) only when all of its inputs are high (1); otherwise, it is high (1).


But, in negative input AND gate means give the input to the AND gate after inverting the actual input and finally it behaves like NOR gate.



#### 4. What is pull-up & pull-down network?

- **Pull-up network:** Uses a resistor to connect a signal to a high voltage (usually Vcc), ensuring the signal defaults to high (logic 1) when no active driver is pulling it low (logic 0).
- **Pull-down network:** Uses a resistor to connect a signal to ground, ensuring the signal defaults to low (logic 0) when no active driver is pulling it high (logic 1).
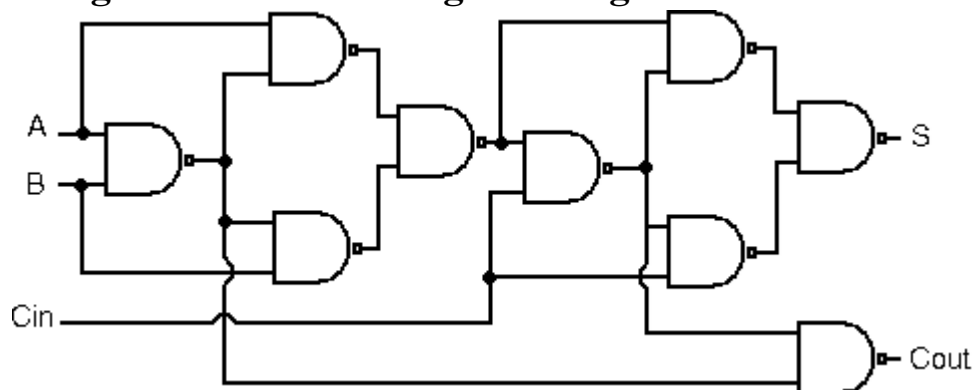
#### 5. Design a full adder using NAND gates ONLY



#### 6. Explain the working of a Full subtractor

A full subtractor is a combinational logic circuit used in digital electronics to perform subtraction of three bits: the minuend (A), the subtrahend (B), and the borrow (Borrow In, Bin). It produces two outputs: the difference (Difference, D) and a borrow output (Borrow Out, Bout) that indicates if a borrow is required for the next higher significant bit in a multi-bit subtraction.

##### Inputs:

- **A (Minuend):** The first operand, typically the larger number.
- **B (Subtrahend):** The second operand, the number to be subtracted from A.
- **Bin (Borrow In):** The borrow input from the previous lower significant bit subtraction.

##### Outputs:

- **D (Difference):** The result of  $A - B - \text{Bin}$ .
- **Bout (Borrow Out):** Indicates if a borrow is needed for the next higher significant bit.

### Truth Table:

The operation of a full subtractor can be summarized with the following truth table:


A	B	Bin	D (Difference)	Bout (Borrow Out)
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

## 7. Difference between Ripple Carry Adder and Carry Look Ahead Adder

The Ripple Carry Adder (RCA) computes the sum of binary numbers sequentially, starting from the least significant bit (LSB) and propagating any carry generated to the next higher bit. This sequential carry propagation introduces delay that increases with the number of bits, causing performance to slow noticeably as the bit width grows. RCA designs are straightforward, involving a series connection of full adder units.

In contrast, the Carry Look Ahead Adder (CLA) precomputes carry signals for each bit position based on input bits. This allows carry signals to be generated in parallel, independent of the addition process. CLA exhibits minimal delay regardless of bit size, making it much faster than RCA for larger adders. However, implementing CLA requires more complex logic to compute and manage these carry signals in parallel, resulting in a more intricate design compared to RCA.
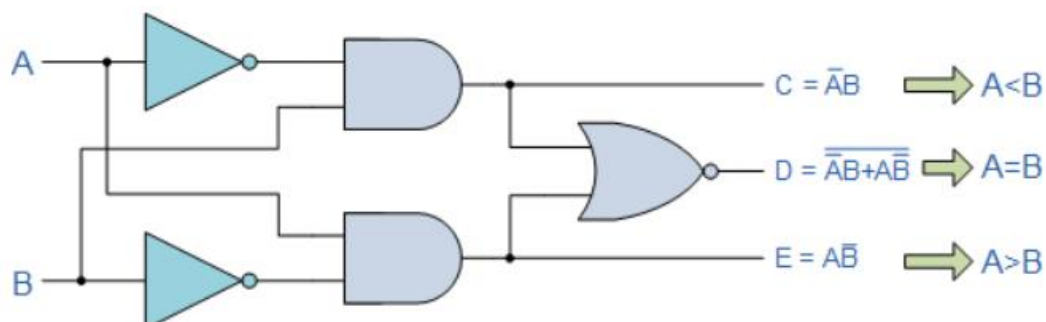
## 8. Explain Comparator with truth table.



Inputs		Outputs		
B	A	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

### 9. Design "Frequency multiplier by 2" circuit.

